



# DCS Lab 5


## AHB interconnect

---

Finite state machine

張芳淇


# Flow Control: ready-valid flow

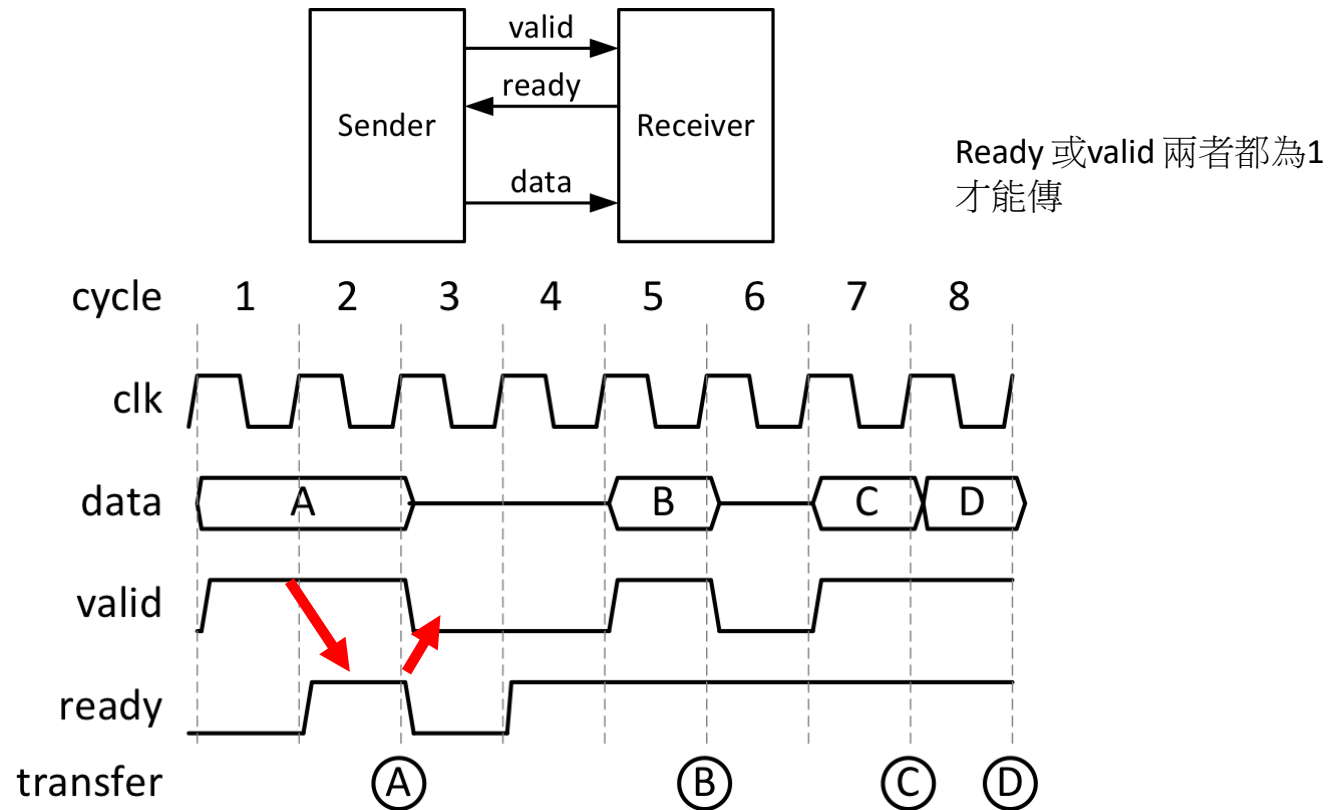


# Handshake process

- Ready before valid / Valid before ready
- Valid with ready


handshake

 

handshake

 


handshake

 

If(valid && ready)

# AHB Interconnect

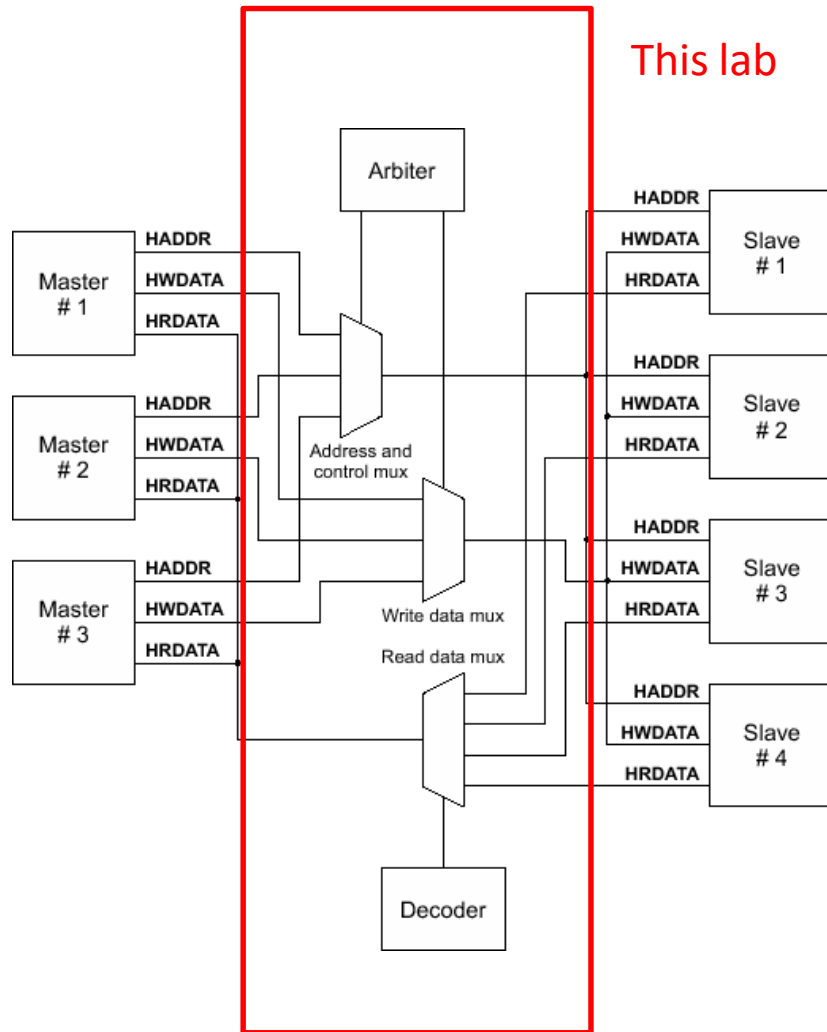


Basic components:

- Master
- Slave
- Arbiter
- Decoder
- Mux

# Lab - block diagram

## Pattern

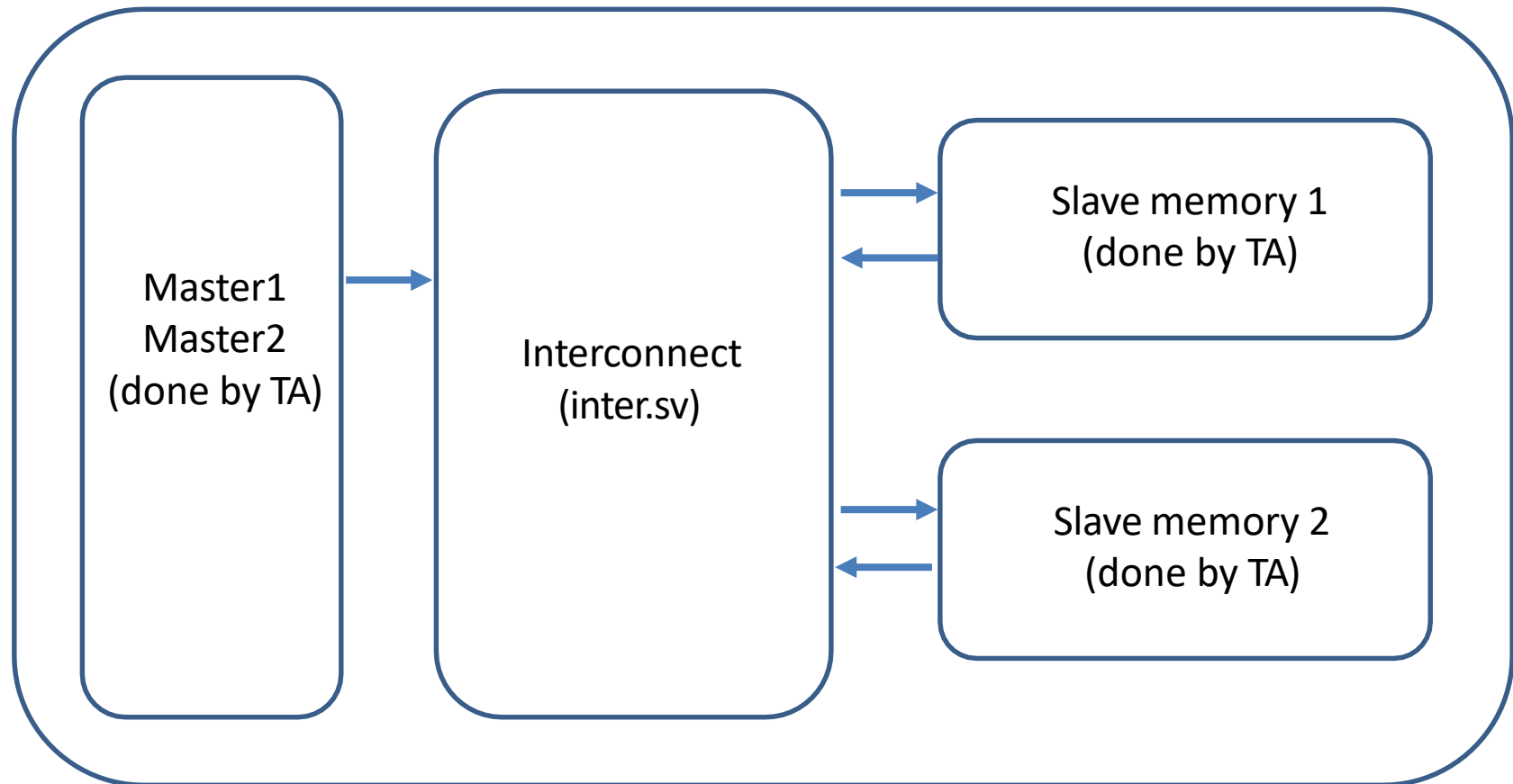

# Lab

- Masters will send input data to interconnect
- You should decode input data for valid, address and value
- Based on **master priority(1->2)**, send data to slave memory
- Output handshake signal

# Lab - decode

- [6:0]data\_in\_1 (from Master1)
- data\_in\_1[6]: 0->slave1 1->slave2
- data\_in\_1[5:3]: address
- data\_in\_1[2:0]: value
- Ex: 7'b0101001 for slave1, addr=5, value=1
- Ex: 7'b1011110 for slave2, addr=3, value=6

# inter.sv

Input Signal	Bit Width	Definition
clk	1	Clock
rst_n	1	Asynchronous active-low reset
in_valid_1	1	in_valid from master1
in_valid_2	1	in_valid from master2
data_in_1	7	Data from master1
data_in_2	7	Data from master2
ready_slave1	1	Ready signal from slave1
ready_slave2	1	Ready signal from slave2




# inter.sv

Output Signal	Bit Width	Definition
valid_slave1	1	valid signal to slave1
valid_slave2	1	valid signal to slave2
addr_out	3	Address you want to write
value_out	3	Value you want to save
handshake_slave1	1	High for 1 cycle after handshake with slave1
handshake_slave2	1	High for 1 cycle after handshake with slave2

# Lab – Arbiter FSM (ref.)

in1 = in\_valid\_1訊號的暫存器

in2 = in\_valid\_2訊號的暫存器

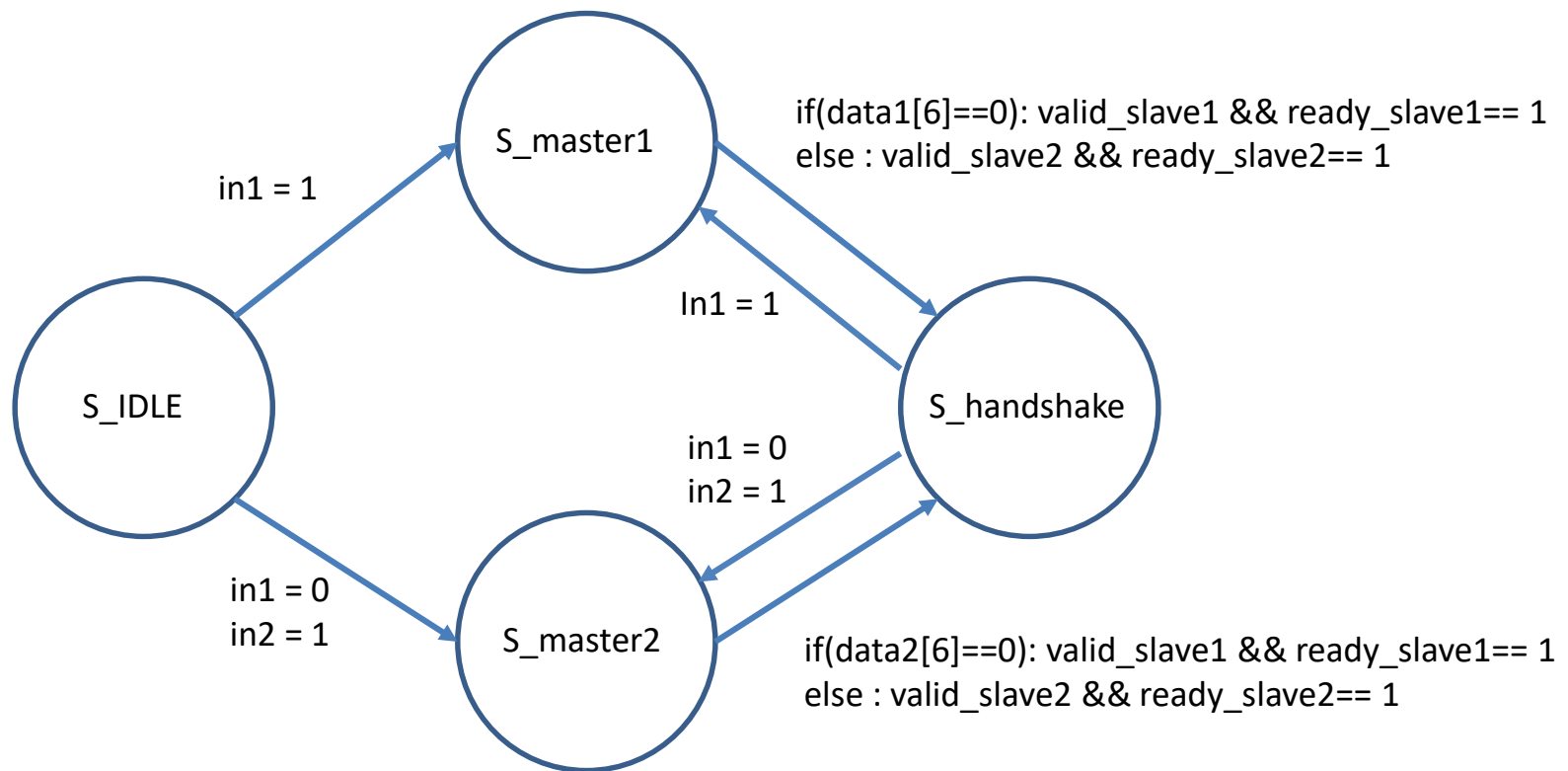


S\_master1 and S\_master2:

- Set valid\_slave
- Set value\_out and addr\_out

# Spec


- 不可以超過30個cycles沒有完成handshake(從invalid或上一次handshake開始數)
- 拉起handshake signal(**only 1 cycle**)後,pattern會檢查 全部slave memory的值，必須依照master priority
- 可參考助教提供的FSM。
- 所有output必須非同步負準位reset。
- Coding style (combination 和 sequential要分開寫否則-5分)
- 01\_RTL 需要PASS。
- 02\_SYN不能有error跟latches。
- 02\_SYN時間timing slack必須為MET。
- 03\_GATE 需要PASS
- 宣告logic/wire/reg/submodule/parameter時，名稱勿包含\*error\*, \*congratulation\*, \*latch\* or \*fail\*等詞，字串裡含有上述關鍵詞也不行，例如"error\_note", "read\_fail"都會造成demo錯誤。(**FAIL!!!!**)

# Waveform

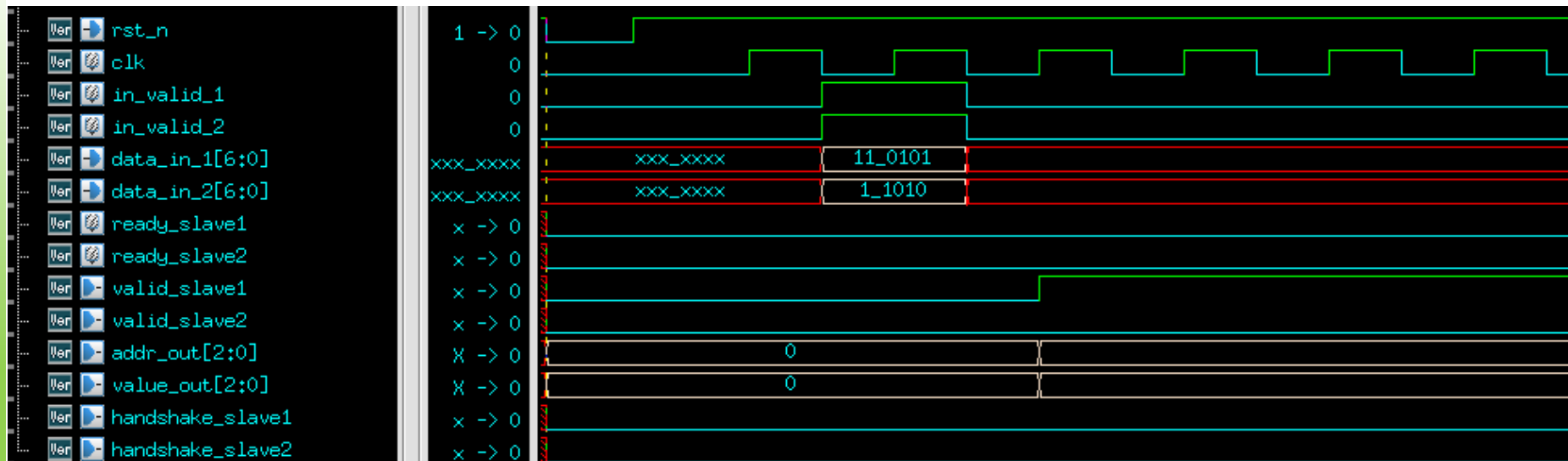


negative trigger asynchronous reset

# Waveform

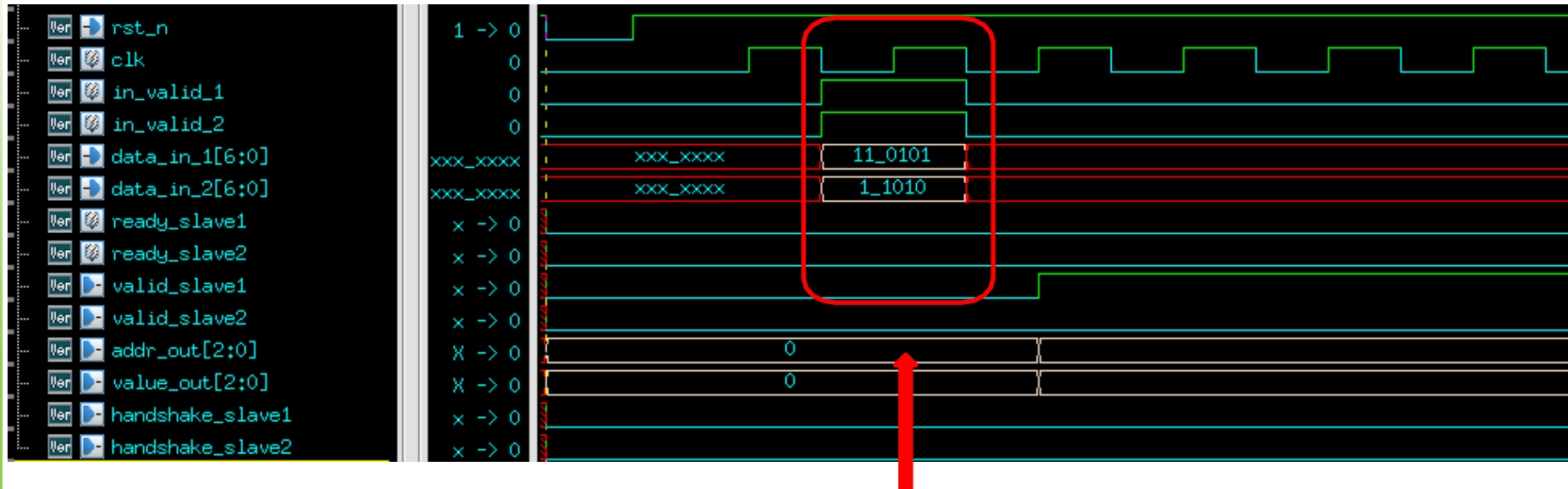

Input data


# Waveform

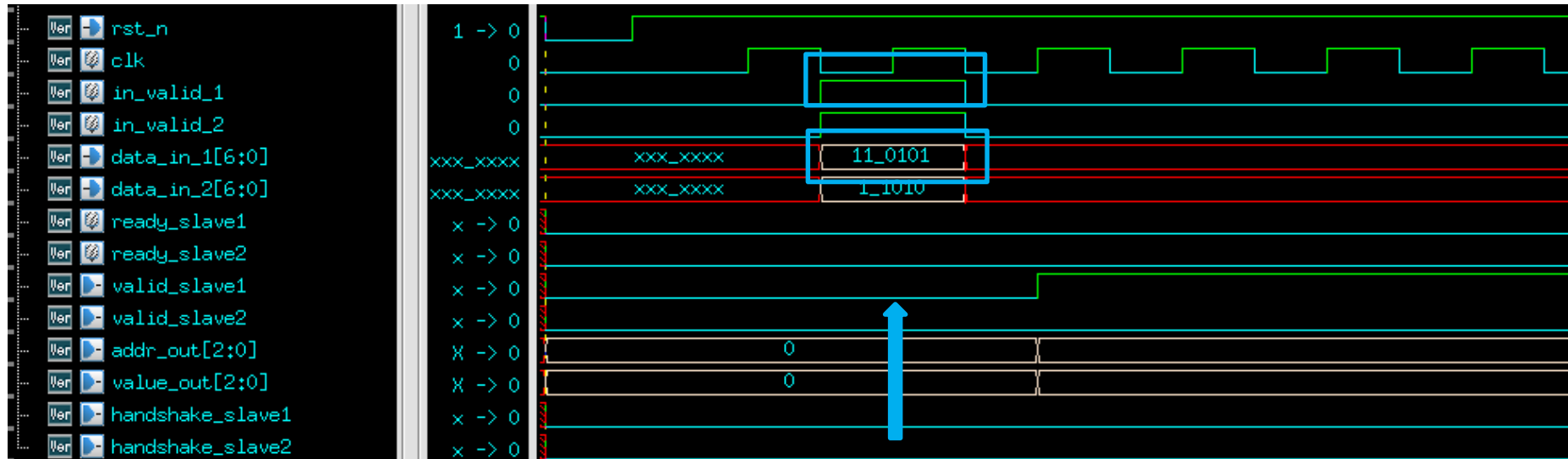

Master1 first


Decode: 0 110 101 => slave1 address:6 value:5

# Waveform

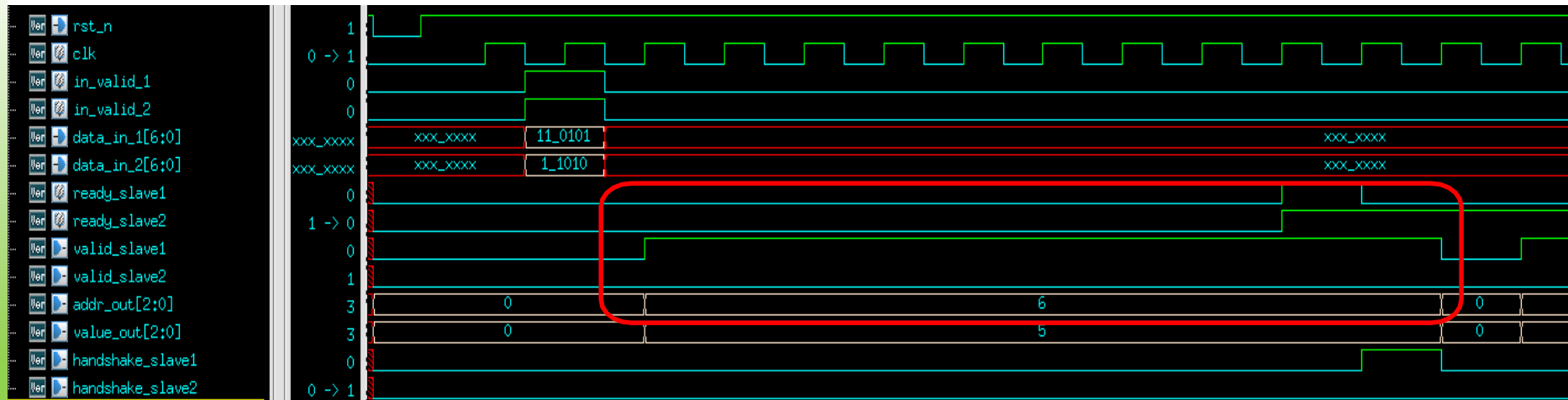


Set valid high, wait slave1 ready

# Waveform

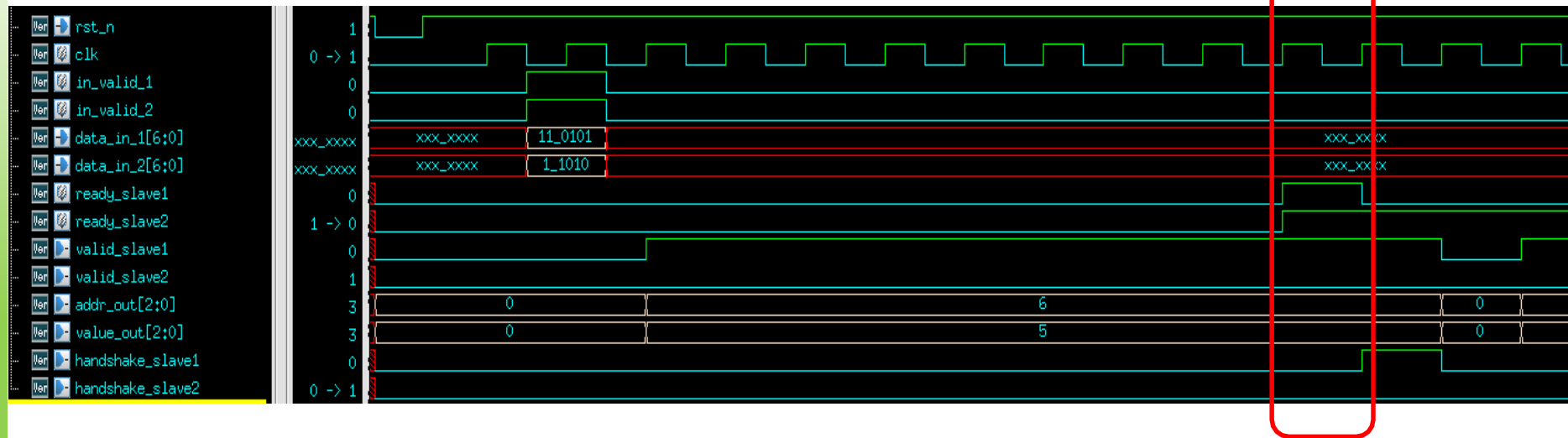




# Waveform

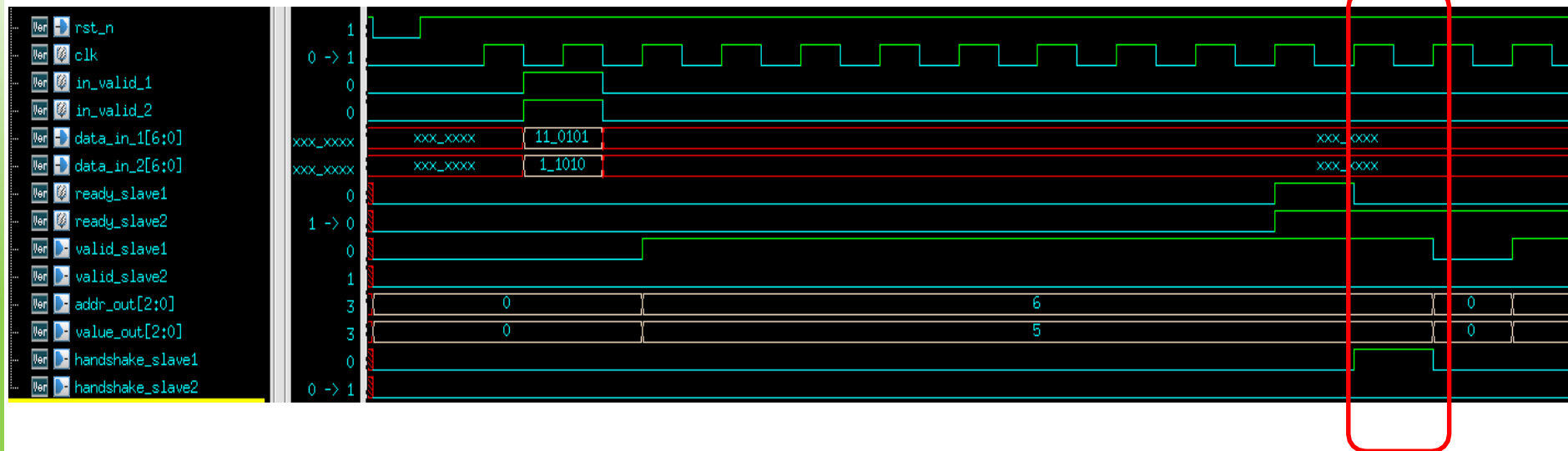

output handshake signal

# Waveform


Continue for Master2

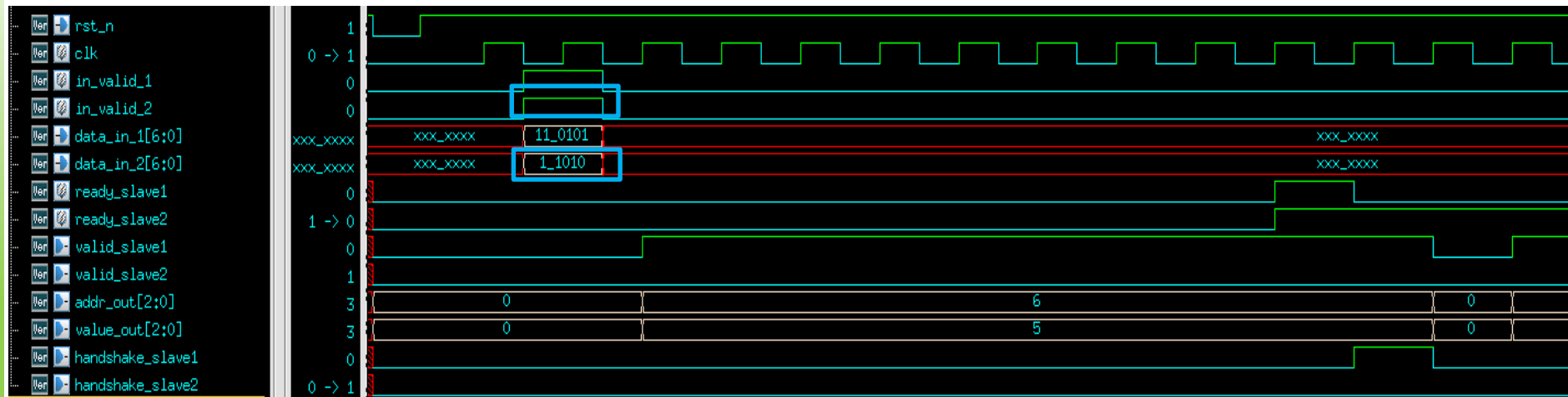

# Waveform

## Pattern 1

## Pattern 2

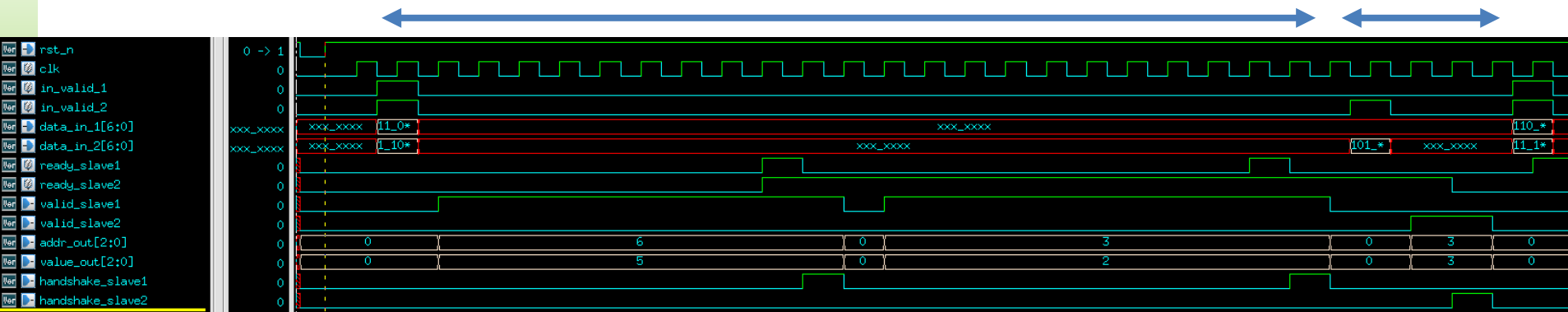

# Command

- `tar -xvf ~dcsta01/Lab05.tar`
- `cd Lab05/01_RTL/`
- Need 02\_SYN
  - No Latch
  - No error
  - No timing violation (MET)
- Need 03\_GATE
- **Separate combinational and sequential blocks**

Demo1: 3/30(四), 16:20:00

Demo2: 3/30(四), 23:59:59

# FSM simple example

```

parameter S_idle = 'd0;
parameter S_master1 = 'd1;
parameter S_master2 = 'd2;
parameter S_handshake = 'd3;
logic [1:0] cur_state, next_state;
//-----
//  YOUR DESIGN
//-----
always_ff @(posedge clk or negedge rst_n) begin
    if(!rst_n)
        cur_state <= S_idle;
    else
        cur_state <= next_state;
end

always_comb begin
    case(cur_state)
        S_idle :
            //statement
        S_master1:
            //statement
        S_master2:
            //statement
        S_handshake:
            //statement
        default: //statement
    endcase
end

```

宣告

state register

next state logic